

BCD Adder

Objective:

- 1- The student use the previous studies in design not start from zero.
- 2- The student knows steps to design circuit.
- 3- How to design adder.

Problem:

You have 2-BCD numbers and you want to get the summation of its.

So


Input: From 0 to 9.

Max number is represented in 4- bit so input is 4-bit for the first number, 4-bit for the second number and one bit for the carry from the previous operation so the input is 9-bit.

Output: Min addition is $0+0+0=0$

Max addition is $9+9+1=19$

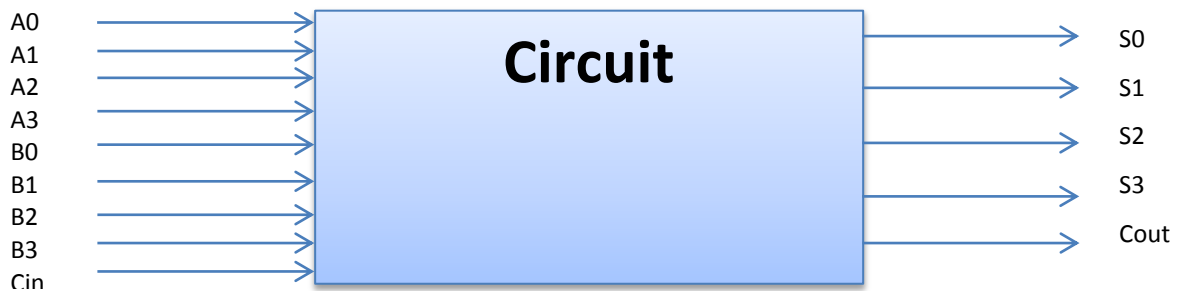So output 4-bit for the first number and 4-bit for the second number but the max number for the second digit is 1 it represented in 4-bit as 0001 so 3-most significant bits can be neglected so the output is 5-bits.



Design:

Design #1:


By using truth table: - we have 9- input so we have 2^9 (512) probability case. So it is impossible to design by this way.

Design #2:

Use 4-bit full adder

Input usually binary as shown

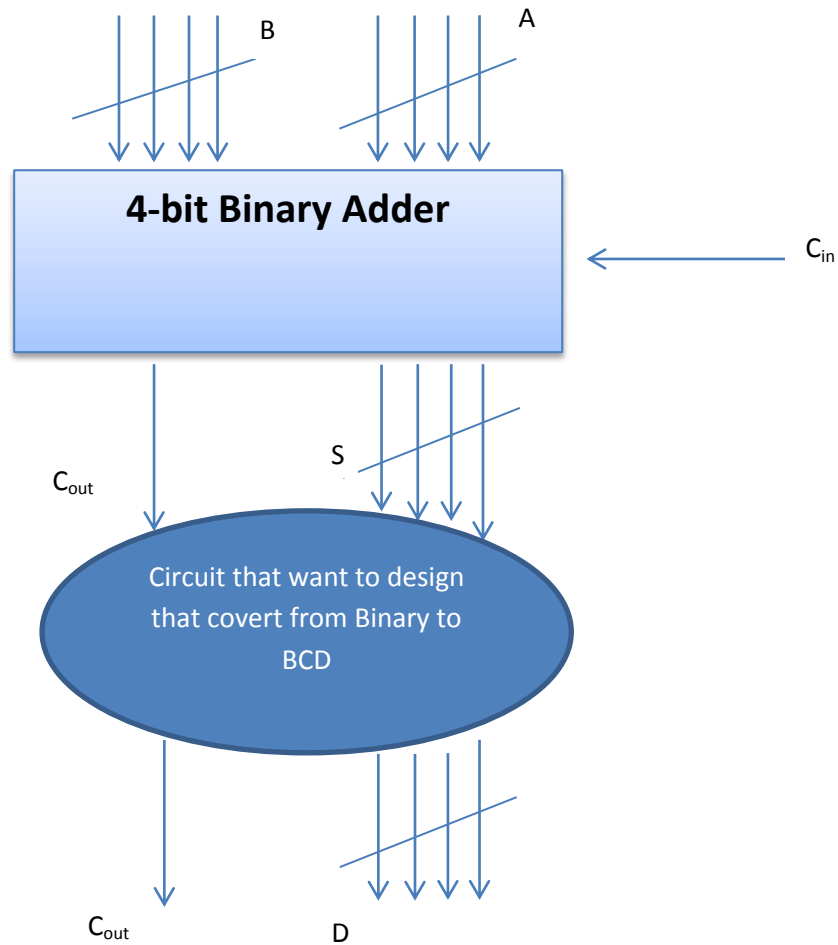If we want to make this 2+7 in BCD 2 represented as $(0010)_{\text{BCD}}$ and 7 as $(0111)_{\text{BCD}}$ but out from the binary adder is binary so we need a circuit that convert from binary to BCD.



C _{out}	S3	S2	S1	S0	digit	C _{out}	D3	D2	D1	D0
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	1	0	0	0	0	1
0	0	0	1	0	2	0	0	0	1	0
0	0	0	1	1	3	0	0	0	1	1
0	0	1	0	0	4	0	0	1	0	0
0	0	1	0	1	5	0	0	1	0	1
0	0	1	1	0	6	0	0	1	1	0
0	0	1	1	1	7	0	0	1	1	1
0	1	0	0	0	8	0	1	0	0	0
0	1	0	0	1	9	0	1	0	0	1
0	1	0	1	0	10	1	0	0	0	0
0	1	0	1	1	11	1	0	0	0	1
0	1	1	0	0	12	1	0	0	1	0
0	1	1	0	1	13	1	0	0	1	1
0	1	1	1	0	14	1	0	1	0	0
0	1	1	1	1	15	1	0	1	0	1
1	0	0	0	0	16	1	0	1	1	0
1	0	0	0	1	17	1	0	1	1	1
1	0	0	1	0	18	1	1	0	0	0
1	0	0	1	1	19	1	1	0	0	1

Design as 5-functions we can deduce them (C_{out}, d3, d2, d1 and d0) by k-map or Boolean algebra.

You can deduce them as min-terms and represented them

So this design may be represented but it too long.

Design #3:

We also use 4-bit binary adder but by notice from the previous table Number from 0 to 9 represented as them but from 10 to 19 represented as following:

1- (01010)₂
(10)₁₀

(10000)_{BCD}
(16)₁₀

2- $(01011)_2$

$(11)_{10}$

:
:
:
:
:
:
:

$(10001)_{BCD}$

$(17)_{10}$

:
:
:
:
:
:
:

10- $(10011)_2$

$(19)_{10}$

:
:
:
:
:
:
:

$(11001)_{BCD}$


$(25)_{10}$

:
:
:
:
:
:
:

Note that the difference between the numbers represented is always 6.



Trick:-

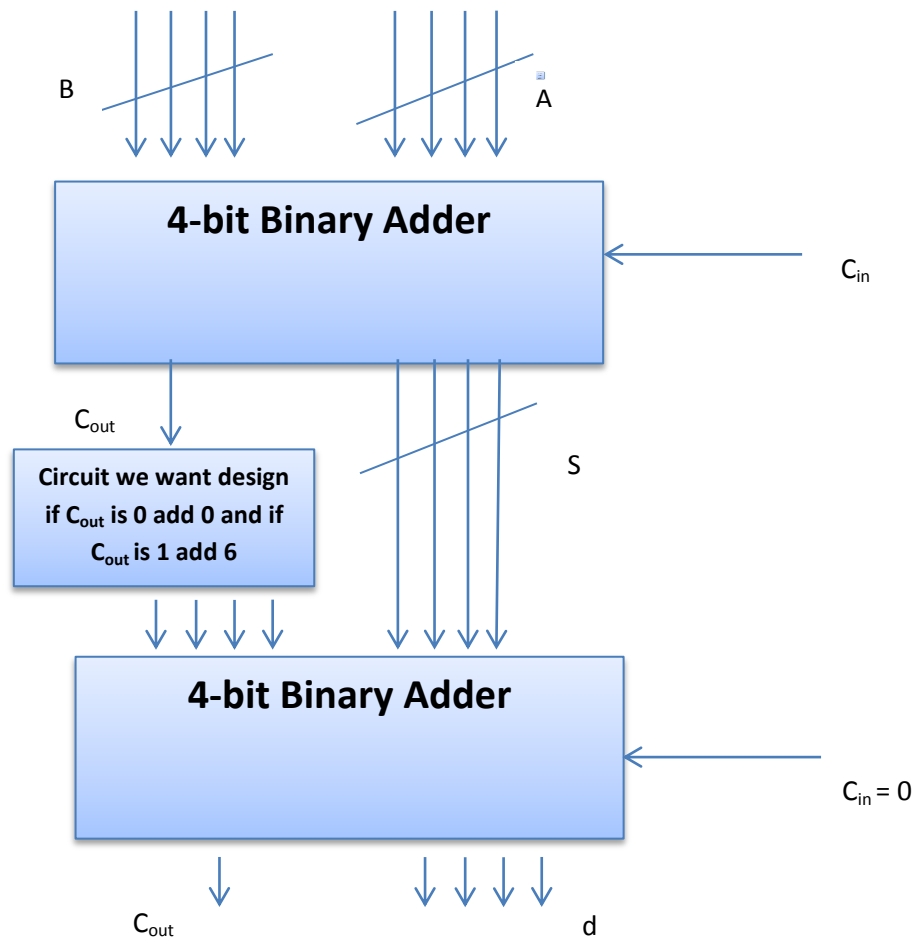If the C_{out} is 0 we add 0 to the binary number from the full adder and if C_{out} is 1 so we add 6.



0	0	0	0	1	1	1	1
0	0	0	0	X	X	X	X
1	1	1	1	X	X	X	X
0	0	1	1	X	X	X	X

$$Z = C_{out} + S3S2 + S3S1$$

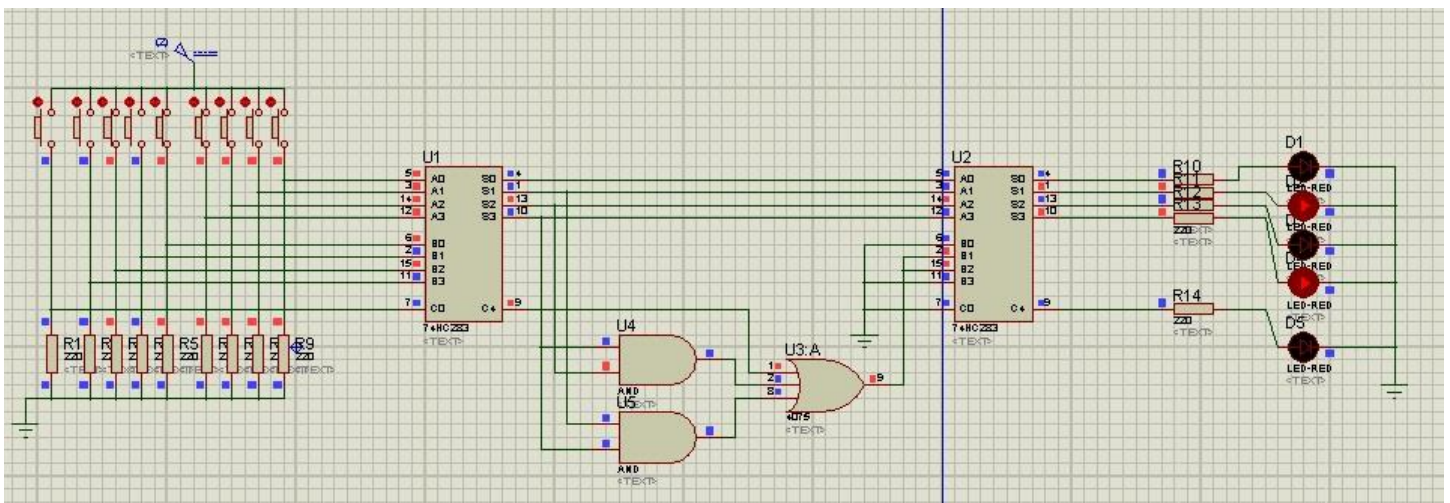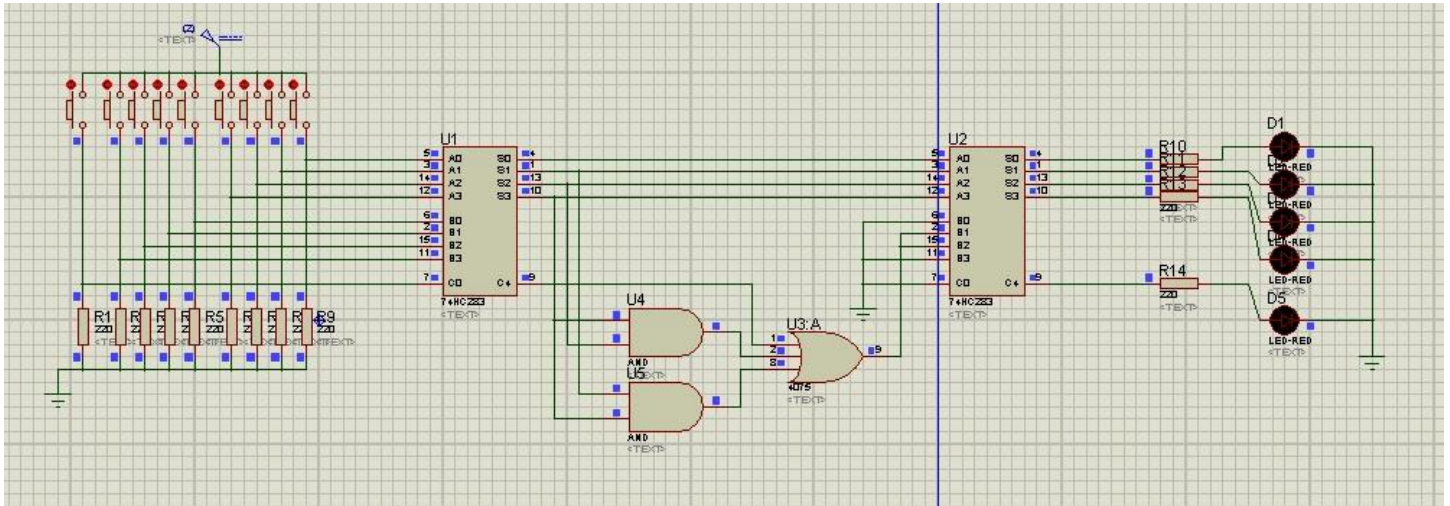

Report:

Design a Circuit to multiply 4*3 bit (analysis –design- hardware)

Prepared by Eng. / Ahmed Osman

Thanks for regards